
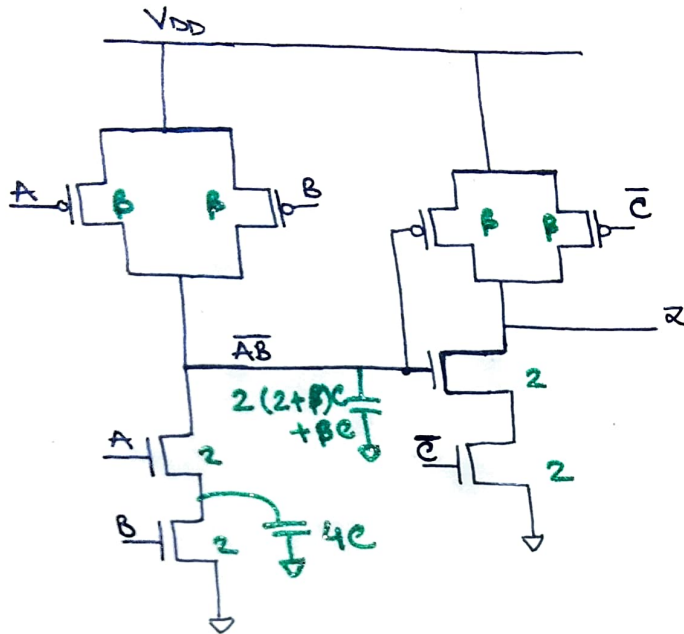


OR

(a), (b), (c)

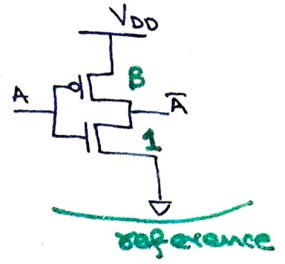

* $t_{PLH} = 0.69 \left\{ \frac{R}{\cancel{R}} \times [2(2+\beta)C + \beta C] \right\} \rightarrow A=1, B=0 \text{ or } A=0, B=1$


* $t_{PHL} = 0.69 \left\{ \frac{R}{2} \times 4C + R \times [2(2+\beta)C + \beta C] \right\} \rightarrow A=1, B=1$

* $t_p = \max \{ t_{PLH}, t_{PHL} \}$
or

* $t_p = \left\{ \frac{t_{PLH} + t_{PHL}}{2} \right\}$


Q6.

(a), (b)

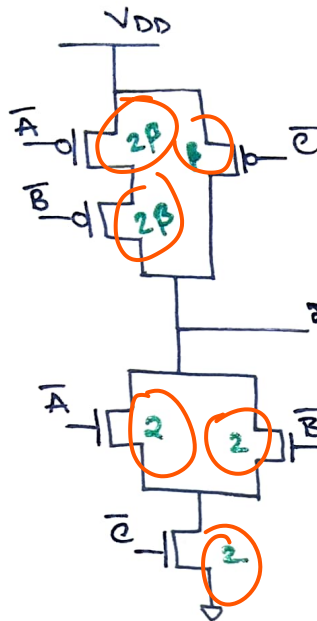

$$Z = (\overline{A+B}) \cdot \overline{C} = \underline{\underline{AB+C}}$$

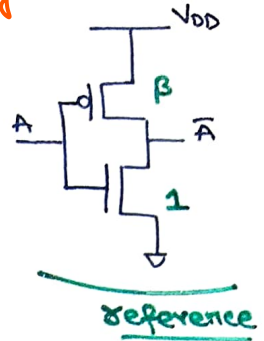give marks even if they directly took $\beta = 2$.




PDN size - 1 mark

PVN size - 1 mark

implementation: 4 marks. if proceeds along correct direction, give appropriate marks

(c)

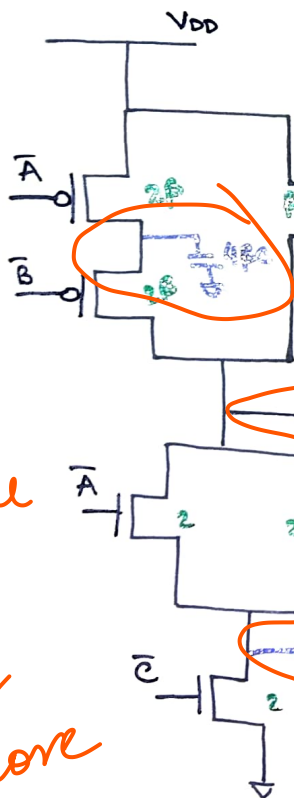

$$= 0.69RC [5P + 4]$$

Worst case $\{A=1, B \neq 1\}$

$$* t_{PLH} = 0.69 \left[\frac{R}{2\beta} \times 4\beta C + R \times (4+3\beta)C \right]$$

$$= 0.69 \left[2 + \frac{4+3\beta}{\beta} \right] RC$$

$$* t_{PHL} = 0.69 \left[\frac{R}{2} \times 6C + R \times (4+3\beta)C \right]$$

$$= 0.69 [3 + 4 + 3\beta] RC$$

$$= 0.69 [7 + 3\beta] RC$$

Worst case $\Rightarrow \{A=0 \text{ \& } C=0\}$
or
 $\{B=0 \text{ \& } C=0\}$

1 mark for correct value of cap.

1 mark for using C1 more delay.



1 mark for final answer.

$$\Rightarrow t_p = \max \{t_{PLH}, t_{PHL}\} \rightarrow \text{worst case}$$

$$\text{or}$$

$$\Rightarrow t_p = \left\{ \frac{t_{PLH} + t_{PHL}}{2} \right\}$$

Q.7] a.]

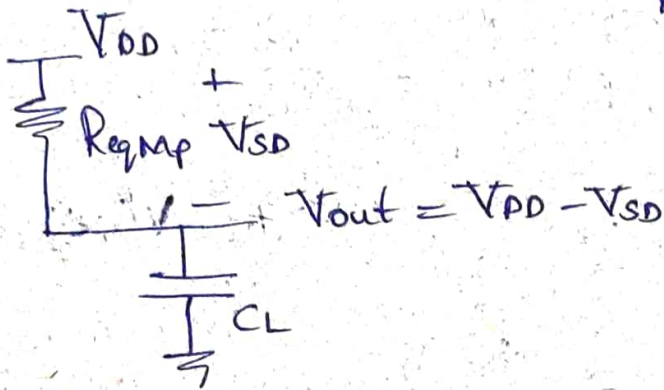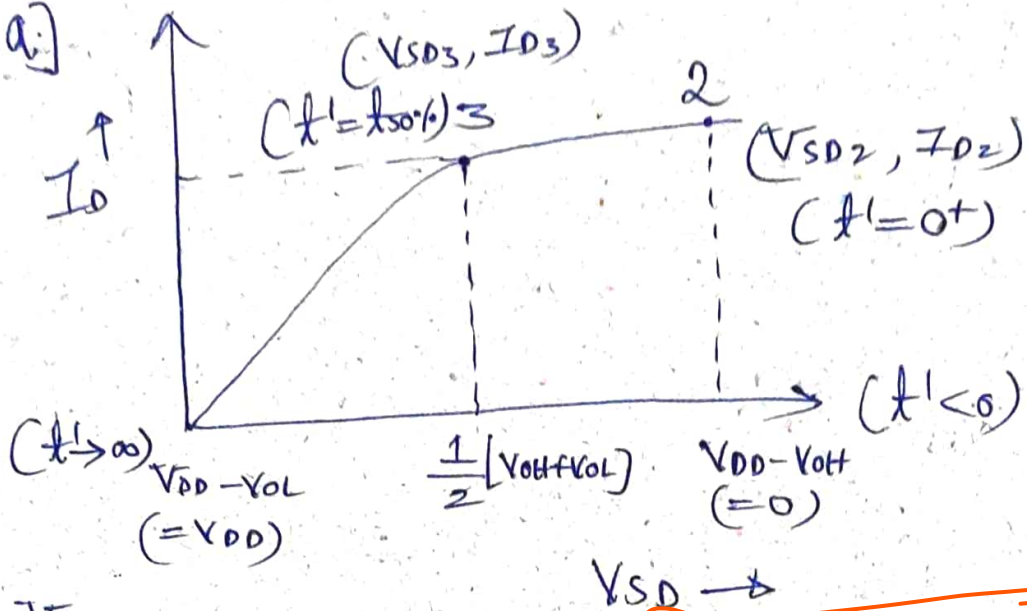

* Minimum Sized Inverter $\Rightarrow WTP = 2k_n$

$$\Rightarrow \text{At } t = 0^+, R_{eq}(0^+) = \frac{V_{SD2}}{I_{D2}}$$

* $V_0 \approx 0V$ [just after $t=0$] and PMOS is in saturation [$\because V_{SD} > V_{SG} - |V_{tp}| \Rightarrow V_0 < V_G + |V_{tp}|$]
 $\Rightarrow 0 < 0 + 0.4$, hence Proved]

$$V_{SD2} = V_{DD} - 0 = 1.8V$$

$$I_{SD2} = \frac{K_P'}{2} \times 2 \times [V_{SG} - |V_{tp}|^2] [1 + \lambda V_{SO}]$$

$$= \frac{150 \times 10^{-6}}{2} \times 2 \cdot [1.8 - 0 - 0.4]^2 [1 + (0.01 \times 1.8)]$$

$$= 0.299 \text{ mA}$$

$$\Rightarrow R_{eq}(0^+) = \frac{1.8}{0.299 \times 10^{-3}} = 6.02 \text{ k}\Omega$$

 $\frac{1}{2}$
$$\frac{1}{2}$$

⇒ $t = 50\%$, $R_{eqMP}(t=50\%) = V_{SD3}/I_{D3}$ and MP is in linear region. $\frac{1}{2}$

$$V_{SD3} = \frac{1}{2} [V_{OH} + V_{OL}] = \frac{1}{2} [1.8] = 0.9V$$

$$I_{D3} = K_P' \cdot \frac{W}{L} \cdot \left[(V_{SG} - |V_{tp}|) V_{SD} - \frac{V_{SD}^2}{2} \right] \times \left\{ 1 + \lambda V_{SD} \right\}$$

$$= 150 \times 10^{-6} \times 2 \times \left[(1.8 - 0 - 0.4) 0.9 - \frac{0.9^2}{2} \right] \times \left\{ 1 + (0.01 \times 0.9) \right\}$$

$$= 258.8085 \mu A$$

$$\therefore R_{eq} [t=50\%] = \frac{0.9 \times 10^3}{258.8085} \Omega = 3.477 K\Omega$$

$$\Rightarrow \text{Total } R_{eqMP} = \frac{1}{2} [6.02K + 3.477K] = 4.7485 K\Omega$$

$$\Rightarrow t_{PLH} = 0.69 C_L R_{eqMP}$$

$$= 0.69 \times 100 \times 10^{-15} \times 4.7485 \times 10^3$$

$$= 0.69 \times 4.7485 \times 10^{-10}$$

$$= 3.276465 \times 10^{-10} \text{ seconds}$$

b) I_{scmax} occurs when $V_{in} = V_m$

$\rightarrow V_m = \frac{V_{DD}}{2} = \frac{1.8V}{2} = 0.9V$

$\rightarrow I_{Dsat} = \frac{K_n}{2} [V_{GS} - V_{tn}]^2 [1 + \lambda V_{DS}]$ in Saturation region.

$$= \frac{300 \times 10^{-6}}{2} [0.9 - 0.4]^2 [1 + 0.01 \times 0.9]$$

$$= 0.037 \text{ mA}$$

$$\therefore I_{scmax} = 0.037 \text{ mA}$$

b) [OR] We get $(I_{sc})_{max}$ when both the Txs are in saturation.

$$\boxed{I_{dsn} = -I_{dsp}} \mid V_{in} = V_m \rightarrow \textcircled{1} \quad \text{You can also go with } I_{dsn} = I_{dsp}$$

$$I_{dsn} = \frac{1}{2} K_n' \frac{W_n}{L_n} [V_m - V_{tn}]^2$$

$$I_{dsp} = \frac{1}{2} K_p' \frac{W_p}{L_p} [V_m - V_{DD} - V_{tp}]^2 \rightarrow \textcircled{2}$$

from $\textcircled{1}$ and $\textcircled{2}$, \rightarrow -ve number

$$\Rightarrow V_m - V_{tn} = \pm \gamma [V_m - V_{DD} - V_{tp}]$$

-ve is correct for $(V_m - V_{tn})$ to be +ve

$$\Rightarrow V_m (1 + \gamma) = V_{tn} + \gamma [V_{DD} + V_{tp}]$$

$$\therefore V_m = \frac{V_{tn} + \gamma [V_{DD} + V_{tp}]}{1 + \gamma}$$

$$\therefore \gamma = \sqrt{\frac{K_p' W_p}{K_n' W_n}}$$

$$V_m = 0.4 + \cancel{1} [1.8 - 0.4]$$

$$1 + \left(\frac{1}{1}\right)$$

$$V_m = \frac{0.9}{0.814} \text{ V} \quad \cancel{I_{sc} \text{ max}} \neq 0.028 \text{ mA}$$

$$\therefore (I_{sc})_{max} = 0.037 \text{ mA}$$

c) We get steep slope for a V_{in} range of " V_{tn} " to " $V_{DD} - |V_{tp}|$ ".

$\frac{1}{2}$

→ At V_{tn} : NMOS in sat and PMOS in linear.

✓ NMOS

$$V_{DS} > V_{GS} - V_{tn}$$

$$\therefore \boxed{V_O > 0V} \rightarrow (1)$$

✓ PMOS

$$V_{SD} < V_{SG} - |V_{tp}|$$

$$V_O > V_{G1} + |V_{tp}|$$

$$V_O > 0.4 + 0.4$$

$$\therefore \boxed{V_O > 0.8V} \rightarrow (2)$$

→ At $V_{DD} - |V_{tp}|$: NMOS in linear and PMOS in saturation.

✓ NMOS

$$V_O < 1.8 - 0.4 - 0.4$$

$$(\because V_{DS} < V_{GS} - V_{tn})$$

$$\therefore \boxed{V_O < 1V} \rightarrow (3)$$

✓ PMOS

$$V_{SD} > V_{SG} - |V_{tp}|$$

$$V_O < V_{G2} + |V_{tp}|$$

$$V_O < V_{DD} - |V_{tp}| + |V_{tp}|$$

$$\therefore \boxed{V_O < 1.8V}$$

→ (4)

Hence, from (1), (2), (3) and (4) we get output range as

$$\boxed{0.8V < V_O < 1V}$$

$\frac{1}{2}$

$$\begin{aligned}
 (M_p)_{SiGe} &= 2.4 (M_p)_{Si} \\
 &= 2.4 \left(\frac{W_p}{L} \right)_{Si} \\
 &= 1.2 W_p L_{min}
 \end{aligned}$$




⇒ to have a symmetric CMOS inverter

$$\left(\frac{W}{L} \right)_n = 1.2 \left(\frac{W}{L} \right)_p$$



one approach would be to choose

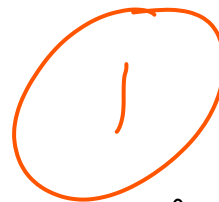- $L_n = L_p = L_{min}$
- $W_p = W_{min} = L_{min}$
- $W_n = 1.2 W_{min} = 1.2 L_{min}$



$$\begin{aligned}
 \Rightarrow \text{area under gate of PMOS} &= W_p \times L_p = L_{min}^2 \\
 \text{area under gate of NMOS} &= W_n \times L_n = 1.2 L_{min}^2
 \end{aligned}$$

$$\Rightarrow \text{total area under gates for 1 MOSFET} = 2.2 L_{min}^2$$

$$\text{—————} 100 \text{ ———} = 220 L_{min}^2 \text{ ———} \textcircled{1}$$

$$\begin{aligned}
 \bullet \text{ chip area available for making gates} \\
 &= 90\% \times 5 \text{ mm}^2 \\
 &= 4.5 \text{ mm}^2 \text{ ———} \textcircled{2}
 \end{aligned}$$

equating ① and ②,

$$220 L_{min}^2 = 4.5 \text{ mm}^2$$

$$\Rightarrow L_{min} = \sqrt{\frac{4.5}{220}} \text{ mm}$$

$$= 143 \mu\text{m}$$



$$= 143 \mu\text{m}$$

⇒ Sizing :

1

PMOS	NMOS
$L = 143 \mu\text{m}$ $W = 143 \mu\text{m}$	$L = 143 \mu\text{m}$ $W = 143 \times 1.2$ $= 171.6 \mu\text{m}$

1